

Keywords: input voltage efficiency, conversion efficiency, input boost, step-down controller, buck controller, charge pump

#### APPLICATION NOTE 1153

# Simple Circuit Boosts a 3V Input and Improves Efficiency

Jul 29, 2002

*Abstract: In this design note a synchronous buck converter, the MAX1967, and a charge pump improve low-input voltage efficiency. The circuit boosts the 3V input to a 5V output. with a 3% rise in efficiency for a 0.35W power savings.*

The [MAX1967](#) is a voltage mode PWM synchronous buck controller that is ideal for a variety of cost-sensitive applications. Fixed 100kHz switching frequency allows cheap aluminum electrolytic capacitors and powdered-iron core magnetics to be used for minimum-cost designs. The MAX1967 has an input range of 2.7V to 28V. A drawback with low-voltage inputs like 3.3V is that efficiency is penalized due to low gate drive for the external MOSFETs, which exhibit higher on-resistance. This application note shows how to improve low input voltage efficiency by boosting the gate drive supply voltage with a simple diode-capacitor charge pump circuit.

In **Figure 1**, a discrete charge pump composed of D1, D2, C1 and C2 boosts the input voltage. The voltage at the IN pin is 2 times the input voltage,  $V_{in}$ . This is fed to the MAX1967's internal linear regulator input to generate a 5V output,  $V_L$ . Thus, the 5V gate drive is provided to the external MOSFET, even with a 3V input. D3 is used to start up the IC during the soft start. Once the IC and the charge pump circuit start to operate,  $V_L$  provides 5V output, which reverses bias diode D3.

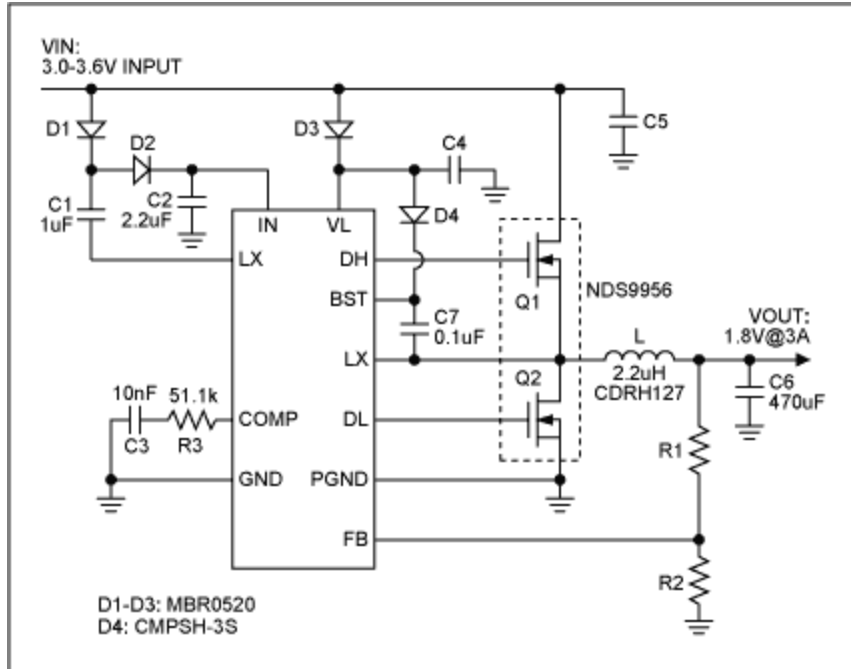


Figure 1. Synchronous buck converter with charge pump.

Figure 2 shows conversion efficiency with 3.0V input and 1.8V output. It is shown that the measured efficiency with the charge pump is 3% higher than that of conventional connection (IN and VL tie to input) at a 2.5A load. This results in 0.35W power savings and reduces heat dissipation.

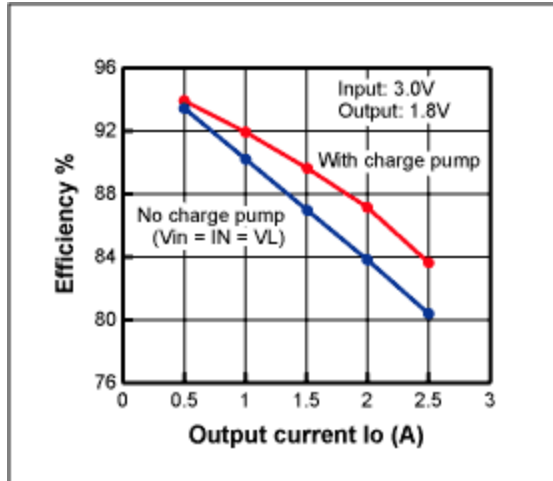


Figure 2. Measured efficiency vs output current.

#### Related Parts

MAX1967

Low-Cost Voltage-Mode PWM Step-Down Controllers

Free Samples

#### More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>  
Other Questions and Comments: <http://www.maximintegrated.com/contact>

---

Application Note 1153: <http://www.maximintegrated.com/an1153>  
APPLICATION NOTE 1153, AN1153, AN 1153, APP1153, Appnote1153, Appnote 1153  
Copyright © by Maxim Integrated Products  
Additional Legal Notices: <http://www.maximintegrated.com/legal>